

ASSIGNMENT -7

Advanced Digital Logic Design

BODDU MOURYA CHANDRA

1002022108

Contents

1) Design Requirements :	3
2) Test Bench Results :	4
Q1) TEXT BOOK EXAMPLE	4
Q2)BRO INSTRUCTION	5
Q3)MUL INSTRUCTION	6
3) Timing Analysis:	7
Q1) TEXT BOOK EXAMPLE	7
Q2) BRO INSTRUCTION INCLUDED	8
Q3)MUL INSTRUCTION INCLUDED	9
4)RTL Diagrams:	10
Q1) TEXT BOOK EXAMPLE	10
Q2)BRO INSTRUCTION	10
Q3)MUL INSTRUCTION	11
5)Verilog Codes :	12
1)RISC_SPM:	12
2) Processing_Unit:	13
3) ALU:	15
4) Eight_Bit_Multiplier_RISC:	18
5) MultControl:	20
6) Address_Register:	22
7) Instruction_Register:	22
8) Register_Unit:	22
9) D_flop:	23
10) Multiplexer_5ch:	23
11) Program_Counter:	24
12) Control_Unit:	25

1) Design Requirements :

- 1) Simulating RISC_SPM code from section 7.3 of Ciletti.
- 2) Incorporating Branch On Overflow instruction (BRO) in RISC_SPM
- 3) Incorporating Multiply (MULT) Instruction in RISC_SPM

2) Test Bench Results :

Q1) TEXT BOOK EXAMPLE

Program:

```
// opcode_src_dest
M2.M2_SRAM.memory[0] = 8'b0000_00_00; // NOP
M2.M2_SRAM.memory[1] = 8'b0101_00_10; // Read 130 to R2
M2.M2_SRAM.memory[2] = 130;
M2.M2_SRAM.memory[3] = 8'b0101_00_11; // Read 131 to R3
M2.M2_SRAM.memory[4] = 131;
M2.M2_SRAM.memory[5] = 8'b0101_00_01; // Read 128 to R1
M2.M2_SRAM.memory[6] = 128;
M2.M2_SRAM.memory[7] = 8'b0101_00_00; // Read 129 to R0
M2.M2_SRAM.memory[8] = 129;


M2.M2_SRAM.memory[9] = 8'b0010_00_01; // Sub R1-R0 to R1

M2.M2_SRAM.memory[10] = 8'b1000_00_00; // BRZ
M2.M2_SRAM.memory[11] = 134; // Holds address for BRZ

M2.M2_SRAM.memory[12] = 8'b0001_10_11; // Add R2+R3 to R3
M2.M2_SRAM.memory[13] = 8'b0111_00_11; // BR
M2.M2_SRAM.memory[14] = 140;

// Load data
M2.M2_SRAM.memory[128] = 6;
M2.M2_SRAM.memory[129] = 1;
M2.M2_SRAM.memory[130] = 2;
M2.M2_SRAM.memory[131] = 0;
M2.M2_SRAM.memory[134] = 139;
M2.M2_SRAM.memory[139] = 8'b1111_00_00; // HALT
M2.M2_SRAM.memory[140] = 9; // Recycle
```

Modelsim Result :

 

Q2)BRO INSTRUCTION


Program :

```
// Add the contents of R2 and R3 untill the R3 hits Overflow
#5
// opcode_src_dest
M2.M2_SRAM.memory[0] = 8'b0000_00_00; // NOP
M2.M2_SRAM.memory[1] = 8'b0101_00_10; // Read 130 to R2
M2.M2_SRAM.memory[2] = 130;
M2.M2_SRAM.memory[3] = 8'b0101_00_11; // Read 131 to R3
M2.M2_SRAM.memory[4] = 131;

M2.M2_SRAM.memory[5] = 8'b0001_10_11; // Add R2+R3 to R3
M2.M2_SRAM.memory[6] = 8'b1001_00_11; // BRO
M2.M2_SRAM.memory[7] = 134;
M2.M2_SRAM.memory[8] = 8'b0111_00_11; // BR
M2.M2_SRAM.memory[9] = 140;

// Load data
M2.M2_SRAM.memory[130] = 10;
M2.M2_SRAM.memory[131] = 10;
M2.M2_SRAM.memory[134] = 139;
M2.M2_SRAM.memory[139] = 8'b1111_00_00; // HALT
M2.M2_SRAM.memory[140] = 5; // Recycle
```

Modelsim Result :

 

Q3)MUL INSTRUCTION


Program:

```
M2.M2_SRAM.memory[0] = 8'b0000_00_00; // NOP
M2.M2_SRAM.memory[1] = 8'b0101_00_10; // Read 130 to R2
M2.M2_SRAM.memory[2] = 130;
M2.M2_SRAM.memory[3] = 8'b0101_00_11; // Read 131 to R3
M2.M2_SRAM.memory[4] = 131;

M2.M2_SRAM.memory[5] = 8'b1010_10_11; // Multiply R2 and R3 and load R2 with Product_LSB and load R3 with product_MSB
M2.M2_SRAM.memory[8] = 8'b0111_00_11; // BR
M2.M2_SRAM.memory[9] = 134;

// Load data
M2.M2_SRAM.memory[130] = 5;
M2.M2_SRAM.memory[131] = 6;
M2.M2_SRAM.memory[134] = 139;
M2.M2_SRAM.memory[139] = 8'b1111_00_00; // HALT
M2.M2_SRAM.memory[140] = 5; // Recycle
```


Modelsim Result :

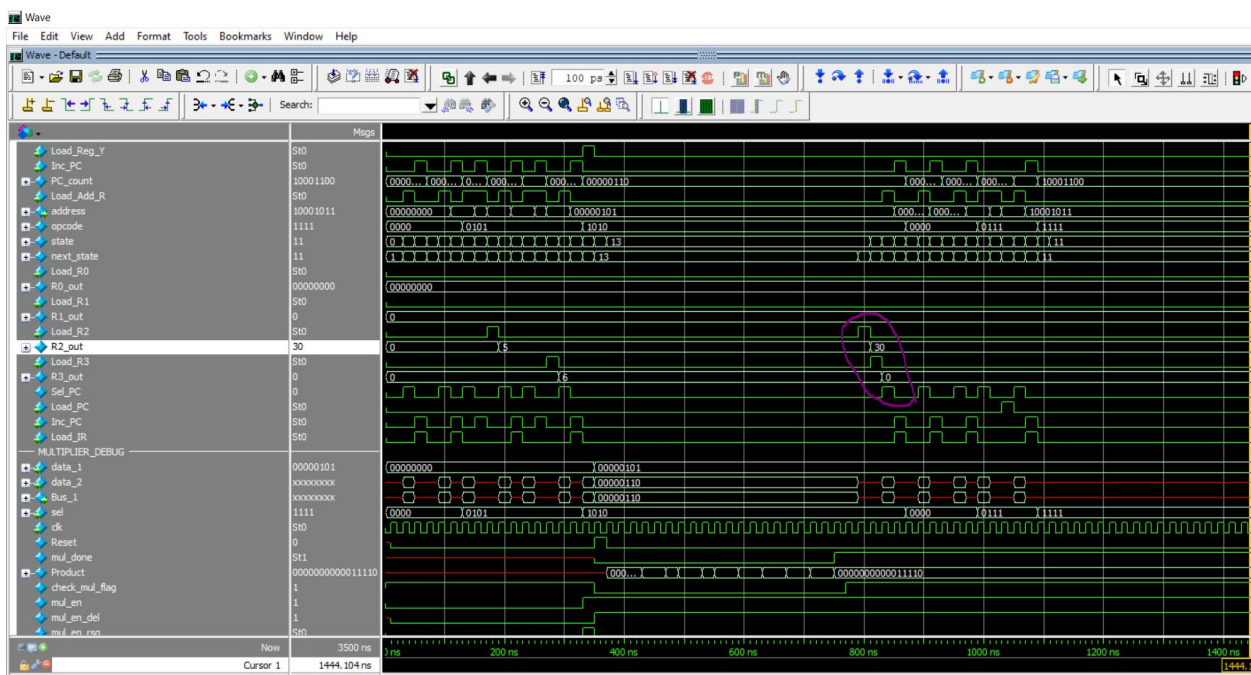


3) Timing Analysis:

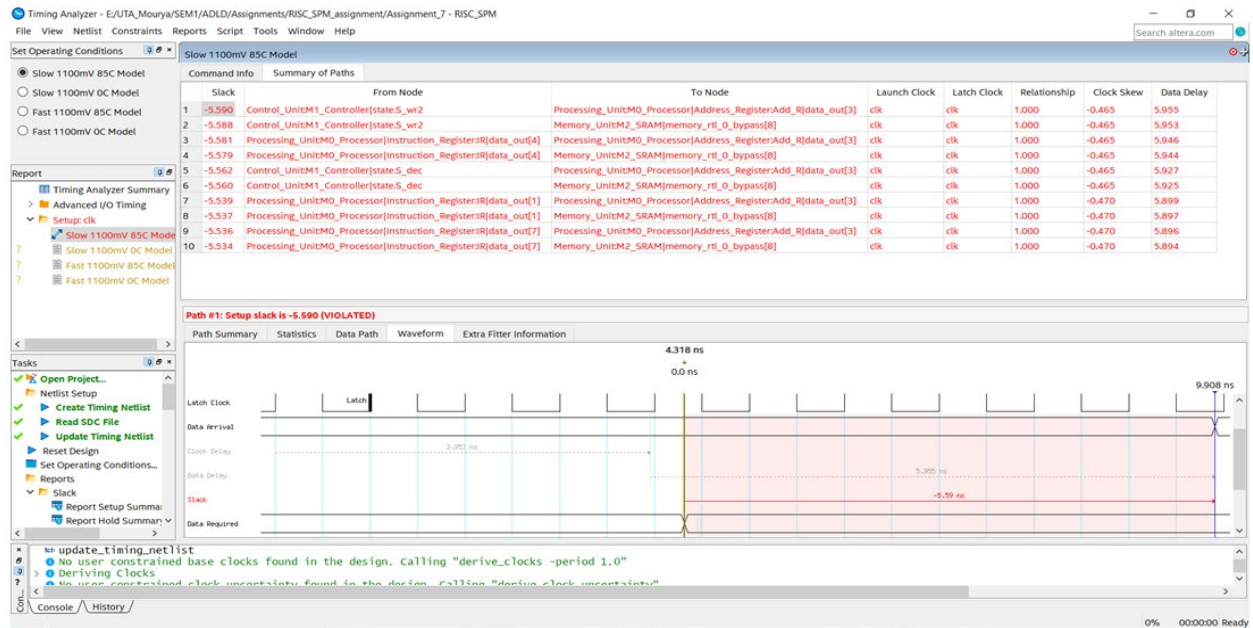Q1) TEXT BOOK EXAMPLE

- The below picture shows the timing analysis with 1ns clock .
- Slack = -5.590 ns




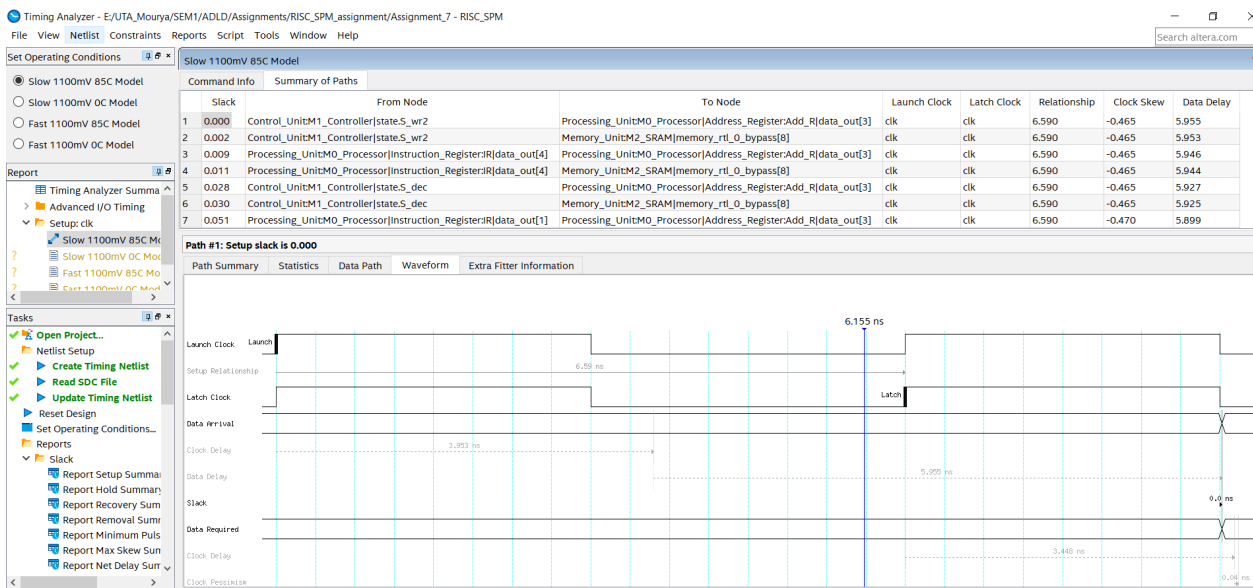- The below picture shows the timing analysis with 6.590 ns clock period.
- Slack = 0 ns ,MAX_Frequency = 1/6.590 GHz =151.7 MHz




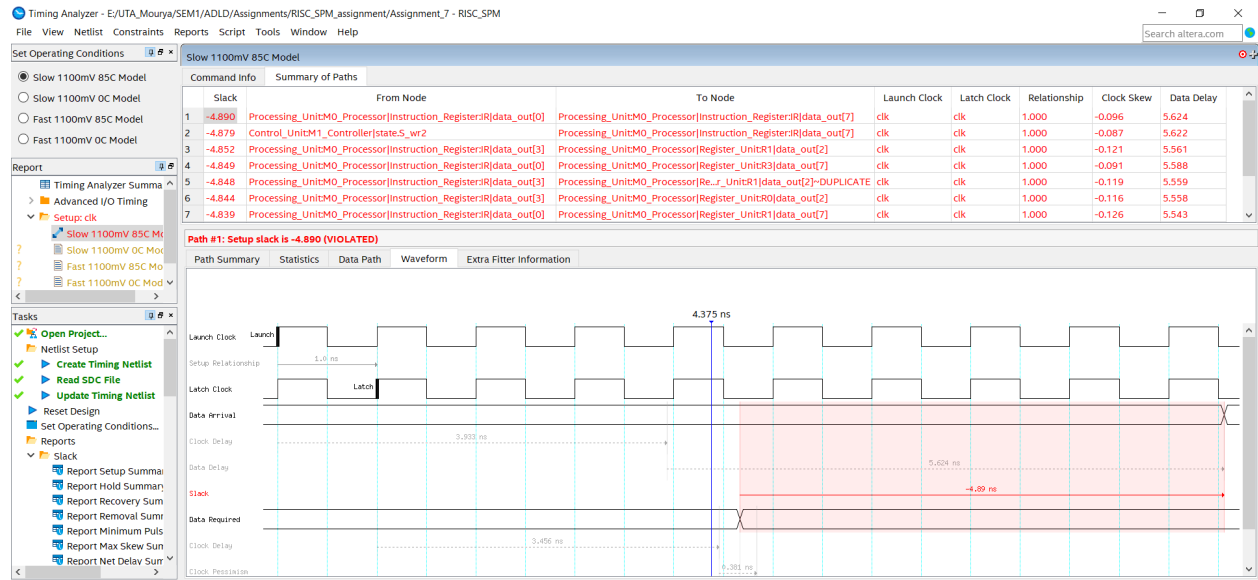Q2) BRO INSTRUCTION INCLUDED

- The below picture shows the timing analysis with 1ns clock .
- Slack = -4.890 ns




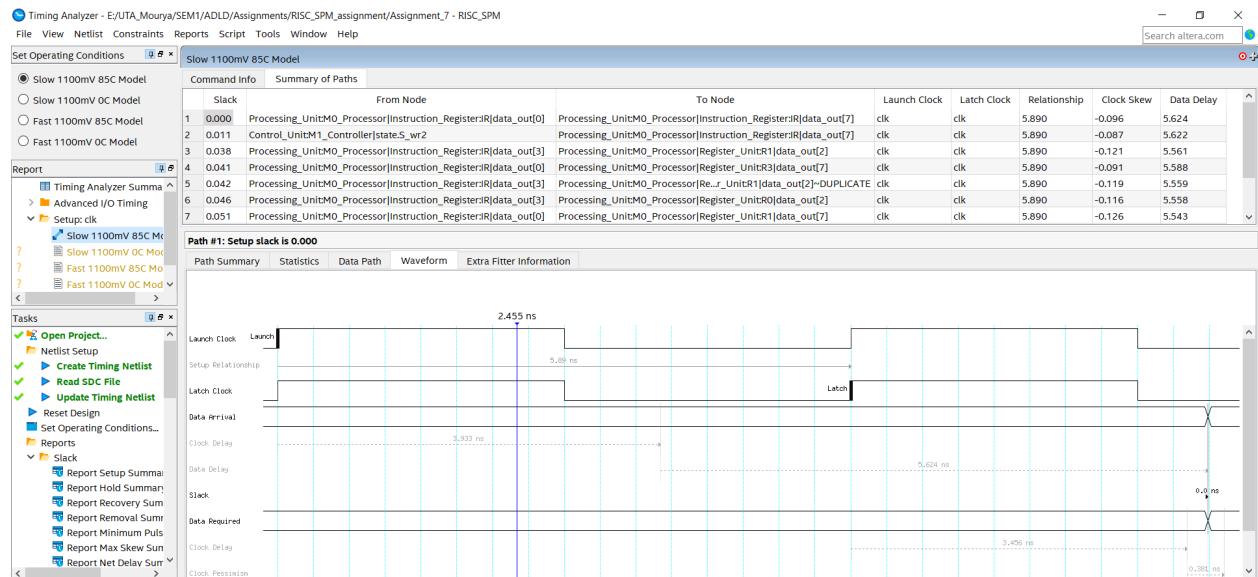- The below picture shows the timing analysis with 5.890 ns clock period.
- Slack = 0 ns ,MAX_Frequency = 1/5.890 GHz =169.7 MHz




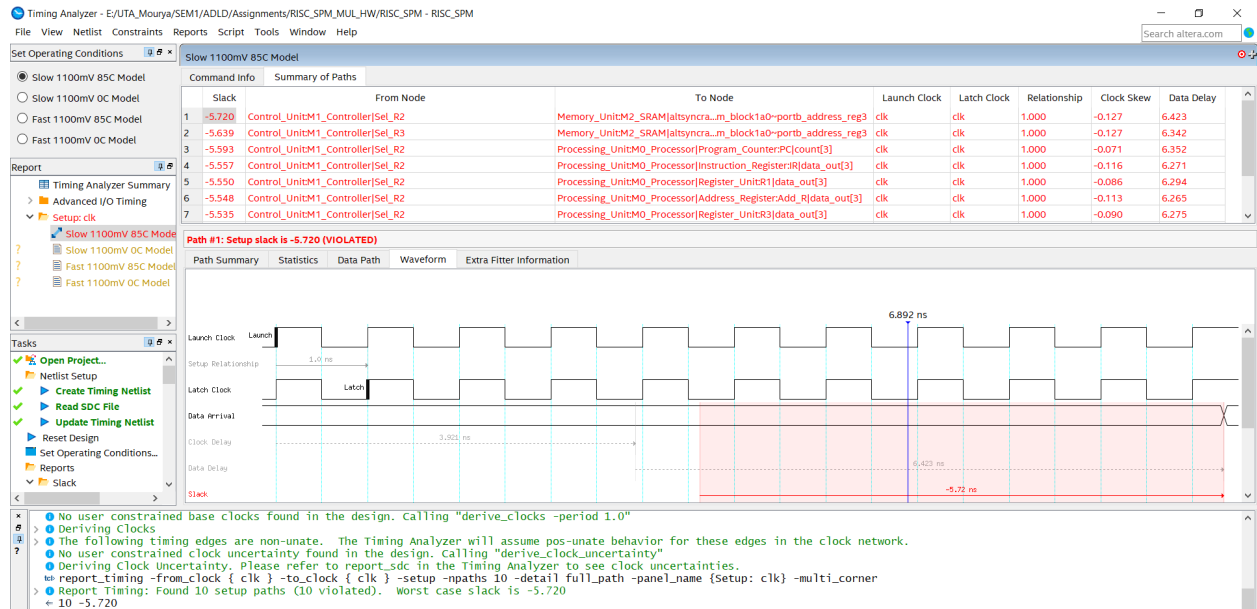Q3)MULT INSTRUCTION INCLUDED

- The below picture shows the timing analysis with 1ns clock .
- Slack = -5.720 ns




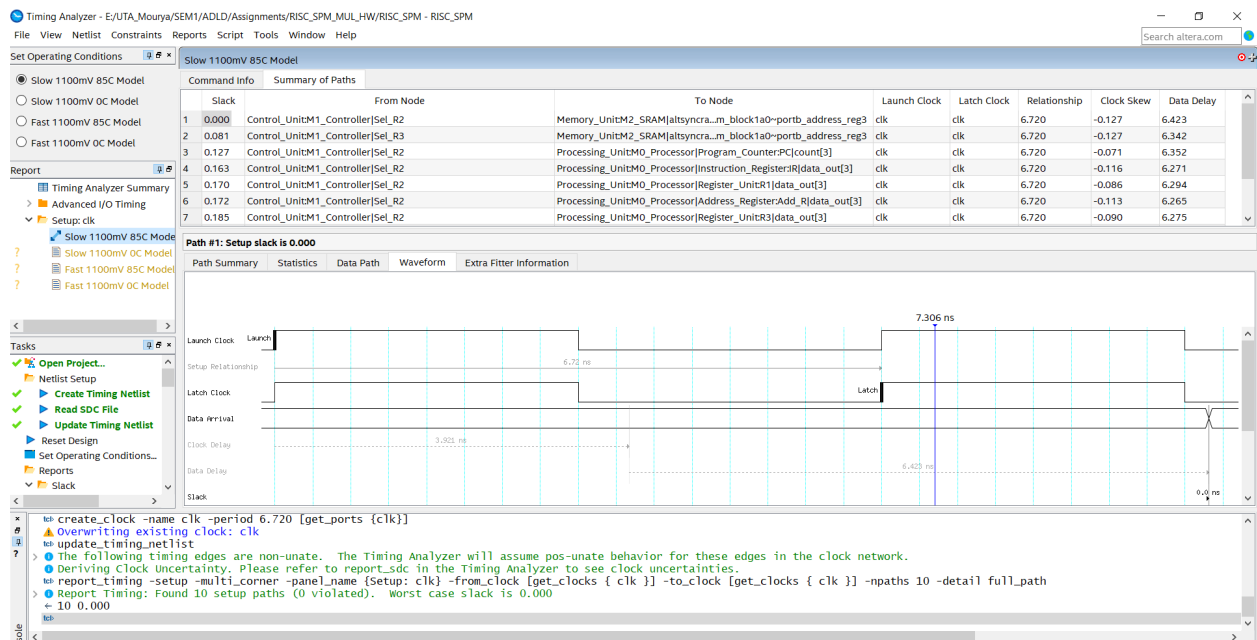- The below picture shows the timing analysis with 6.590 ns clock period.
- Slack = 0 ns ,MAX_Frequency = 1/6.720 GHz =148.8 MHz




4)RTL Diagrams:


Q1) TEXT BOOK EXAMPLE

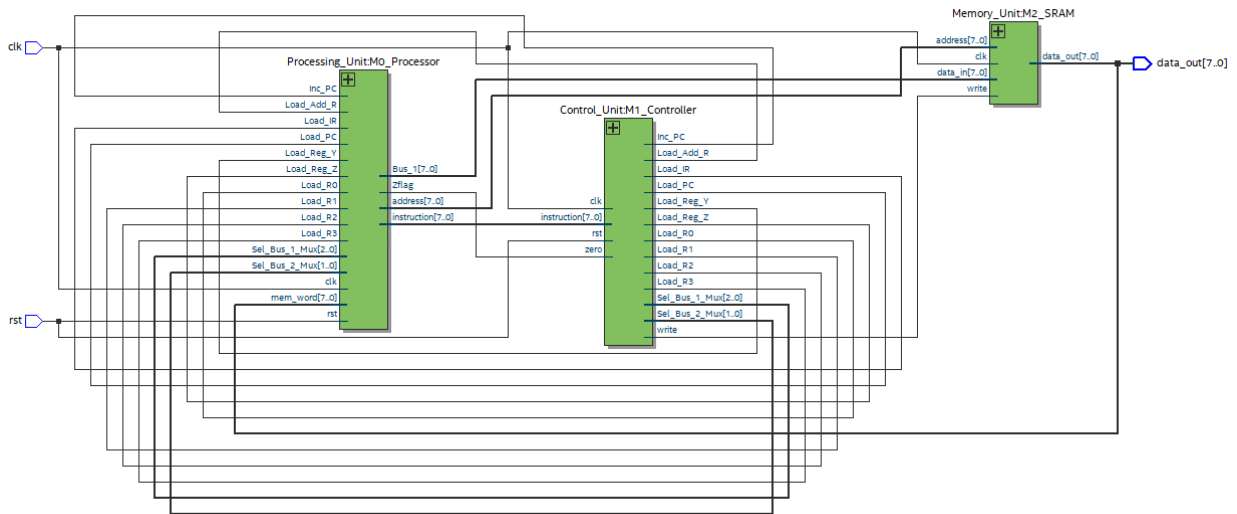

Q2) BRO INSTRUCTION

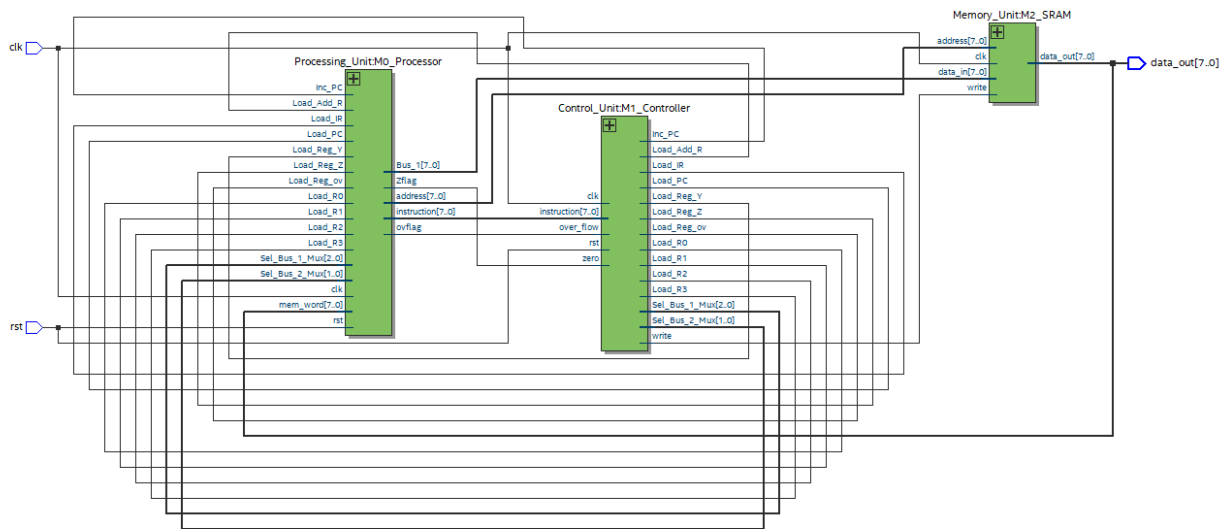

Q3)MULT INSTRUCTION

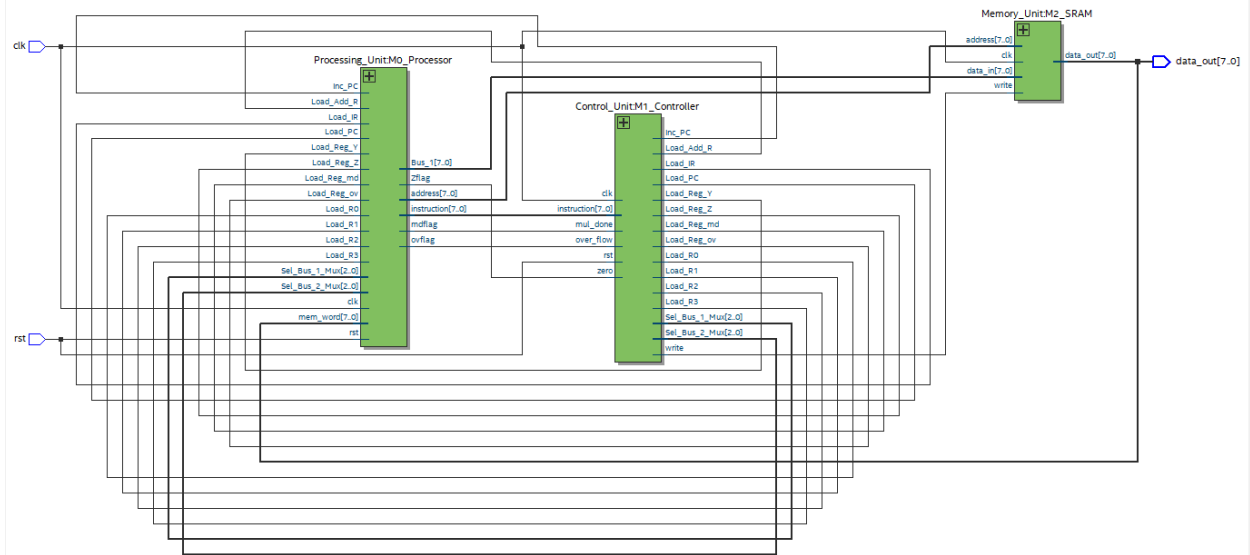

5) Verilog Codes :

1) RISC_SPM:

```
module RISC_SPM (clk, rst, data_out);
    parameter word_size = 8;
    parameter Sel1_size = 3;
    parameter Sel2_size = 3;
    wire [Sel1_size-1: 0] Sel_Bus_1_Mux;
    wire [Sel2_size-1: 0] Sel_Bus_2_Mux;

    input clk, rst;
    output [word_size-1: 0] data_out;

    assign data_out = mem_word ;

    // Data Nets
    wire zero, over_flow, mul_done;
    wire [word_size-1: 0] instruction, address, Bus_1, mem_word;

    // Control Nets
    wire Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Load_IR;
    wire Load_Add_R, Load_Reg_Y, Load_Reg_Z, Load_Reg_ov, Load_Reg_md;
    wire write;

    Processing_Unit M0_Processor (instruction, zero, over_flow, mul_done, address, Bus_1, mem_word,
    Load_R0, Load_R1,
    Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR, Load_Add_R, Load_Reg_Y,
    Load_Reg_Z, Load_Reg_ov, Load_Reg_md, Sel_Bus_2_Mux, clk, rst);

    Control_Unit M1_Controller (Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC,
    Sel_Bus_1_Mux, Sel_Bus_2_Mux, Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,
    Load_Reg_ov, Load_Reg_md,
    write, instruction, zero, over_flow, mul_done, clk, rst);

    Memory_Unit M2_SRAM (
    .data_out(mem_word),
    .data_in(Bus_1),
    .address(address),
    .clk(clk),
    .write(write) );

endmodule
```

2) Processing_Unit:

```
module Processing_Unit (instruction, Zflag,ovflag, mdflag,address, Bus_1, mem_word, Load_R0,
Load_R1, Load_R2,
    Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,
Load_Reg_ov,Load_Reg_md,
    Sel_Bus_2_Mux, clk, rst);

    parameter word_size = 8;
    parameter op_size = 4;
    parameter Sel1_size = 3;
    parameter Sel2_size = 3;

    output [word_size-1: 0]      instruction, address, Bus_1      ;
    output                      mdflag                          ;
    output                      ovflag                          ;
    output                      Zflag                          ;

    input [word_size-1: 0]      mem_word                      ;
    input                      Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC ;
    input [Sel1_size-1: 0] Sel_Bus_1_Mux                      ;
    input [Sel2_size-1: 0] Sel_Bus_2_Mux                      ;
    input                      Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,Load_Reg_ov,Load_Reg_md;
    input                      clk, rst                      ;

    wire                      Load_R0, Load_R1, Load_R2, Load_R3  ;
    wire [word_size-1: 0] Bus_2                      ;
    wire [word_size-1: 0] R0_out, R1_out, R2_out, R3_out      ;
    wire [word_size-1: 0] PC_count, Y_value, alu_out,mul_LSB_byte,mul_MSB_byte      ;
    wire                      alu_zero_flag                ;
    wire                      alu_overflow_flag            ;
    wire                      alu_mul_done_flag            ;
    wire [op_size-1 : 0]      opcode = instruction [word_size-1: word_size-op_size] ;

    Register_Unit      R0      (R0_out, Bus_2, Load_R0, clk, rst);
    Register_Unit      R1      (R1_out, Bus_2, Load_R1, clk, rst);
    Register_Unit      R2      (R2_out, Bus_2, Load_R2, clk, rst);
    Register_Unit      R3      (R3_out, Bus_2, Load_R3, clk, rst);
    Register_Unit      Reg_Y (Y_value, Bus_2, Load_Reg_Y, clk, rst);

    D_flop      Reg_md      (mdflag, alu_mul_done_flag, Load_Reg_md, clk, rst);
    D_flop      Reg_ov (ovflag, alu_overflow_flag, Load_Reg_ov, clk, rst)      ;
    D_flop      Reg_Z      (Zflag, alu_zero_flag, Load_Reg_Z, clk, rst)      ;
    Address_Register      Add_R      (address, Bus_2, Load_Add_R, clk, rst)  ;
    Instruction_Register      IR      (instruction, Bus_2, Load_IR, clk, rst)  ;
    Program_Counter      PC      (PC_count, Bus_2, Load_PC, Inc_PC, clk, rst);
    Multiplexer_5ch      Mux_1 (Bus_1, R0_out, R1_out, R2_out, R3_out, PC_count, Sel_Bus_1_Mux);
```

```

    Multiplexer_5ch Mux_2(Bus_2, alu_out, Bus_1, mem_word,mul_LSB_byte,mul_MSB_byte,
Sel_Bus_2_Mux)          ;
    Alu_RISC        ALU (alu_mul_done_flag,alu_overflow_flag,alu_zero_flag,
alu_out,mul_LSB_byte,mul_MSB_byte, Y_value, Bus_1, opcode,clk)      ;

Endmodule

```

3) ALU:

```
module Alu_RISC (alu_mul_done_flag, alu_overflow_flag, alu_zero_flag,
alu_out, mul_LSB_byte, mul_MSB_byte, data_1, data_2, sel, clk);
    parameter word_size = 8;
    parameter op_size = 4;
    // Opcodes
    parameter NOP      = 4'b0000          ;
    parameter ADD      = 4'b0001          ;
    parameter SUB      = 4'b0010          ;
    parameter AND      = 4'b0011          ;
    parameter NOT      = 4'b0100          ;
    parameter RD       = 4'b0101          ;
    parameter WR       = 4'b0110          ;
    parameter BR       = 4'b0111          ;
    parameter BRZ      = 4'b1000          ;
    parameter BRO      = 4'b1001          ;
    parameter MULT     = 4'b1010          ;

    output                alu_overflow_flag    ;
    output                alu_zero_flag        ;
    output                alu_mul_done_flag    ;
    output [word_size-1: 0] alu_out            ;
    output [word_size-1: 0] mul_LSB_byte       ;
    output [word_size-1: 0] mul_MSB_byte       ;
    input  [word_size-1: 0] data_1, data_2      ;
    input  [op_size-1: 0]   sel                 ;
    input                                clk      ;

    reg    [word_size-1: 0] alu_out            ;
    reg    [word_size-1: 0] Multiplicand       ;
    reg    [word_size-1: 0] Multiplier        ;
    reg                                Reset     ;
    wire                                mul_done ;
    reg                                mul_en    ;
    reg                                mul_en_del ;
    wire                                mul_en_rsg ;
    wire [(2*word_size)-1: 0] Product        ;
    reg                                check_mul_flag;

    //ZERO FLAG
    assign alu_zero_flag = ~|alu_out;

    //OVERFLOW FLAG
    assign alu_overflow_flag = (data_1[word_size - 1] & data_2[word_size - 1] &
~alu_out[word_size - 1]) | (~data_1[word_size - 1] & ~data_2[word_size - 1] & alu_out[word_size - 1])
    ;

    //MUL_DONE_FLAG
```

```

assign alu_mul_done_flag    =    mul_done    ;

initial
begin
    check_mul_flag <=    1'b1    ;
    mul_en         <=    1'b0    ;
end

always @ (sel or data_1 or data_2)
begin
    case (sel)
        NOP: begin alu_out = 0; end
        ADD: begin alu_out = data_1 + data_2; mul_en = 0 ; end // Reg_Y + Bus_1
        SUB: begin alu_out = data_2 - data_1; mul_en = 0 ; end
        AND: begin alu_out = data_1 & data_2; mul_en = 0 ; end
        NOT: begin alu_out = ~ data_2; mul_en = 0 ; end // Gets data from Bus_1
        MULT: mul_en = 1 ;
        default: alu_out = 0 ;
    endcase
end

always @(posedge clk)
begin
    mul_en_del    <=    mul_en ;
end

assign mul_en_rsg    = mul_en & ~(mul_en_del)    ;

always @(posedge clk)
begin
    if(mul_en_rsg == 1'b1 && check_mul_flag == 1'b1)
    begin
        Reset                <=    1'b1    ;
        check_mul_flag        <=    1'b0    ;
    end
    else if(mul_done == 1'b1)
    begin
        check_mul_flag        <=    1'b1    ;
        Reset                  <=    1'b0    ;
    end
    else
        Reset                  <=    1'b0    ;
end

assign mul_LSB_byte    =    Product[7:0]    ;
assign mul_MSB_byte    =    Product[15:8]    ;

```



```

Eight_Bit_Multiplier_RISC MULTIPLIER
(
    .Clock(clk),
    .Reset(Reset) ,
    .Multiplicand(data_1) ,
    .Multiplier(data_2) ,
    .Product(Product) ,
    .mul_done(mul_done)
);

Endmodule

```

4) Eight_Bit_Multiplier_RISC:

//Multiplier. Verilog behavioral model.

```
module Eight_Bit_Multiplier_RISC
(
    input          Clock,
    input          Reset ,
    input  [7:0]    Multiplicand ,
    input  [7:0]    Multiplier   ,
    output [15:0]    Product      ,
    output          mul_done
);

reg  [7:0]  RegQ  ; // Q register
reg  [16:0] RegA  ;// A register
reg  [16:0] RegM  ; // M register
reg  [2:0]  Count ; // 3-bit iteration counter

wire  C0, Start, Add, Shift, sub, sub_flag ;

assign Product = {RegA[7:0],RegQ} ;

// 3-bit counter for #iterations
always @(posedge Clock)
if (Start == 1)
    Count <= 3'b00 ; // clear in Start state
else if (Shift == 1)
    Count <= Count + 1 ; // increment in Shift state

assign C0 = Count[2] & Count[1] & Count[0] ; // detect count = 7

// Multiplicand register (load only)
always @(posedge Clock)
    if (Start == 1)
        RegM <= {{8{Multiplicand[7]}},Multiplicand} ;

// Multiplier register (load, shift)
always @(posedge Clock)
    if (Start == 1)
        RegQ <= Multiplier ; // load in Start state
    else if (Shift == 1)
        RegQ <= {RegA[0],RegQ[7:1]} ; // shift in Shift state

// Accumulator register (clear, load, shift)
always @(posedge Clock)
    if (Start == 1)
        RegA <= 16'd0 ;
    else if(sub == 1)
```

```

        RegA <= RegA - RegM ;           //subtract sub stae
    else if (Add == 1)
        RegA <= RegA + RegM ;           // load in Add state
    else if(Shift == 1) // shift in Shift state
        RegA <= RegA >> 1 ;

// Instantiate controller module

MultControl Ctrl
(
    .Clock(Clock),
    .Reset(Reset),
    .Q0(RegQ[0]),
    .C0(C0),
    .Start(Start),
    .Add(Add) ,
    .sub(sub) ,
    .Shift(Shift),
    .Halt(mul_done)
);

Endmodule

```

5) MultControl:

//Multiplier controller. Verilog behavioral model.

module MultControl

```
(  
    input Clock, Reset, Q0, C0,      //declare inputs  
    output Start, Add,sub, Shift, Halt //declare outputs  
);
```

```
reg [5:0] state;      //five states (one hot –one flip-flop per state)
```

```
//one-hot state assignments for five states
```

```
parameter StartS=6'b000001, TestS=6'b000010, AddS=6'b000100, ShiftS=6'b001000,  
HaltS=6'b010000,subS=6'b100000    ;
```

```
// State transitions on positive edge of Clock or Resets
```

```
always @(posedge Clock, posedge Reset)
```

```
if (Reset==1)
```

```
    state <= StartS      ;           //enter StartS state on Reset
```

```
else
```

```
//change state on Clock
```

```
case (state)
```

```
StartS:
```

```
    state <= TestS      ;           // StartS to TestS
```

```
TestS:
```

```
    if (Q0 == 1 && C0 == 1)
```

```
        state <= subS      ;
```

```
    else if(Q0 == 1)
```

```
        state <= AddS      ;           // TestS to AddS if Q0=1
```

```
    else
```

```
        state <= ShiftS    ;           // TestS to ShiftS if Q0=0
```

```
AddS:
```

```
    state <= ShiftS    ;           // AddS to ShiftS
```

```
subS:
```

```
    state <= ShiftS    ;           // subS to ShiftS
```

```
ShiftS:
```

```
    if (C0)
```

```
        state <= HaltS      ;           // ShiftS to HaltS if C0=1
```

```
    else
```

```
        state <= TestS      ;           // ShiftS to TestS if
```

```
C0=0
```

```
HaltS:
```

```
    state <= HaltS      ;           // stay in HaltS
```

```
endcase
```

```

// Moore model - activate one output per state
assign Start    = state[0]    ; // Start=1 in state StartS, else 0
assign Add      = state[2]    ; // Add=1 in state AddS, else 0
assign Shift    = state[3]    ; // Shift=1 in state ShiftS, else 0
assign Halt     = state[4]    ; // Halt=1 in state HaltS, else 0

assign sub      = state[5]    ;

endmodule

```

6) Address_Register:

```
module Address_Register (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] data_out ;
    input [word_size-1: 0] data_in ;
    input load, clk, rst ;
    reg [word_size-1: 0] data_out ;

    always @ (posedge clk or negedge rst)
        if (rst == 0)
            data_out <= 0 ;
        else if (load)
            data_out <= data_in ;

endmodule
```

7) Instruction_Register:

```
module Instruction_Register (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] data_out ;
    input [word_size-1: 0] data_in ;
    input load ;
    input clk, rst ;
    reg [word_size-1: 0] data_out ;

    always @ (posedge clk or negedge rst)
        if (rst == 0)
            data_out <= 0 ;
        else if (load)
            data_out <= data_in ;

endmodule
```

8) Register_Unit:

```
module Register_Unit (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] data_out ;
    input [word_size-1: 0] data_in ;
    input load ;
    input clk, rst ;
    reg [word_size-1: 0] data_out ;
```

```

always @ (posedge clk or negedge rst)
  if (rst == 0)
    data_out <= 0 ;
  else if (load)
    data_out <= data_in ;

endmodule

```

9) D_flop:

```

module D_flop (data_out, data_in, load, clk, rst);
  output      data_out;
  input       data_in;
  input       load;
  input       clk, rst;
  reg        data_out;

  always @ (posedge clk or negedge rst)
    if (rst == 0)
      data_out <= 0 ;
    else if (load == 1)
      data_out <= data_in ;

endmodule

```

10) Multiplexer_5ch:

```

module Multiplexer_5ch (mux_out, data_a, data_b, data_c, data_d, data_e, sel);
  parameter word_size = 8;
  output [word_size-1: 0] mux_out
  ;
  input  [word_size-1: 0] data_a, data_b, data_c, data_d, data_e ;
  input  [2: 0]          sel
  ;

  assign mux_out = (sel == 0) ? data_a: (sel == 1)
    ? data_b : (sel == 2)
    ? data_c: (sel == 3)
    ? data_d : (sel == 4)
    ? data_e : 'bx;

endmodule

```

11) Program_Counter:

```
module Program_Counter (count, data_in, Load_PC, Inc_PC, clk, rst);
  parameter word_size = 8;
  output [word_size-1: 0] count;
  input [word_size-1: 0] data_in;
  input Load_PC, Inc_PC;
  input clk, rst;
  reg [word_size-1: 0] count;

  always @ (posedge clk or negedge rst)
    if (rst == 0)
      count <= 0;
    else if (Load_PC)
      count <= data_in;
    else if (Inc_PC)
      count <= count + 1;

endmodule
```


12) Control_Unit:

```
module Control_Unit (
    Load_R0, Load_R1,
    Load_R2, Load_R3,
    Load_PC, Inc_PC,
    Sel_Bus_1_Mux, Sel_Bus_2_Mux,
    Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z, Load_Reg_ov, Load_Reg_md,
    write, instruction, zero, over_flow, mul_done, clk, rst);

    parameter word_size = 8, op_size = 4, state_size = 4;
    parameter src_size = 2, dest_size = 2, Sel1_size = 3, Sel2_size = 3;
    // State Codes
    parameter S_idle = 0, S_fet1 = 1, S_fet2 = 2, S_dec = 3;
    parameter S_ex1 = 4, S_rd1 = 5, S_rd2 = 6, S_ex2 = 12, mul_done_wait = 13, LD_MUL_MSB = 14;
    parameter S_wr1 = 7, S_wr2 = 8, S_br1 = 9, S_br2 = 10, S_halt = 11;
    // Opcodes
    parameter NOP = 0, ADD = 1, SUB = 2, AND = 3, NOT = 4, MULT = 10;
    parameter RD = 5, WR = 6, BR = 7, BRZ = 8, BRO = 9;
    // Source and Destination Codes
    parameter R0 = 0, R1 = 1, R2 = 2, R3 = 3;

    output Load_R0, Load_R1, Load_R2, Load_R3;
    output Load_PC, Inc_PC;
    output [Sel1_size-1:0] Sel_Bus_1_Mux;
    output Load_IR, Load_Add_R;
    output Load_Reg_Y, Load_Reg_Z, Load_Reg_ov, Load_Reg_md;
    output [Sel2_size-1:0] Sel_Bus_2_Mux;
    output write;
    input [word_size-1:0] instruction;
    input zero;
    input over_flow;
    input mul_done;
    input clk, rst;

    reg [state_size-1:0] state, next_state;
    reg Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC;
    reg Load_IR, Load_Add_R, Load_Reg_Y;
    reg Sel_ALU, Sel_Bus_1, Sel_Mem, Sel_mul_LSB, Sel_mul_MSB;
    reg Sel_R0, Sel_R1, Sel_R2, Sel_R3, Sel_PC;
    reg Load_Reg_Z, write, Load_Reg_ov, Load_Reg_md;
    reg err_flag;

    wire [op_size-1:0] opcode = instruction [word_size-1: word_size - op_size];
    wire [src_size-1:0] src = instruction [src_size + dest_size - 1: dest_size];
    wire [dest_size-1:0] dest = instruction [dest_size - 1:0];
    reg temp = 0;

    // Mux selectors
```

```

assign Sel_Bus_1_Mux[Sel1_size-1:0] = Sel_R0 ? 0:
    Sel_R1 ? 1:
    Sel_R2 ? 2:
    Sel_R3 ? 3:
    Sel_PC ? 4: 3'bx; // 3-bits, sized number

assign Sel_Bus_2_Mux[Sel2_size-1:0] = Sel_ALU ? 0:
    Sel_Bus_1 ? 1:
    Sel_Mem ? 2:
    Sel_mul_LSB ? 3:
    Sel_mul_MSB ? 4: 3'bx;

always @ (posedge clk or negedge rst) begin: State_transitions
    if (rst == 0) state <= S_idle; else state <= next_state; end

//always @ (posedge clk or state or opcode or zero) begin: Output_and_next_state
always @ (posedge clk ) begin: Output_and_next_state
//always @ (posedge clk ) begin: Output_and_next_state
    Sel_R0 = 0; Sel_R1 = 0; Sel_R2 = 0; Sel_R3 = 0; Sel_PC = 0;
    Load_R0 = 0; Load_R1 = 0; Load_R2 = 0; Load_R3 = 0; Load_PC = 0;
    Load_IR = 0; Load_Add_R = 0; Load_Reg_Y = 0; Load_Reg_Z = 0;
Load_Reg_ov = 0; Load_Reg_md = 0 ;
    Inc_PC = 0 ;
    Sel_Bus_1 = 0 ;
    Sel_ALU = 0 ;
    Sel_Mem = 0 ;
    Sel_mul_LSB = 0 ;
    Sel_mul_MSB = 0 ;
    write = 0 ;
    err_flag = 0 ; // Used for de-bug in simulation
    next_state = state ;

case (state)
    S_idle:
        next_state = S_fet1;

    S_fet1: begin
        next_state = S_fet2;
        Sel_PC = 1;
        Sel_Bus_1 = 1;
        Load_Add_R = 1;
    end

    S_fet2: begin
        next_state = S_dec;
        Sel_Mem = 1;
        Load_IR = 1;
        Inc_PC = 1;

```

end

S_dec: case (opcode)

NOP: next_state = S_fet1;

ADD, SUB, AND: begin

next_state = S_ex1;

Sel_Bus_1 = 1;

Load_Reg_Y = 1;

case (src)

R0: Sel_R0 = 1;

R1: Sel_R1 = 1;

R2: Sel_R2 = 1;

R3: Sel_R3 = 1;

default : err_flag = 1;

endcase

end // ADD, SUB, AND

NOT: begin

next_state = S_fet1;

Load_Reg_Z = 1;

Sel_Bus_1 = 1;

Sel_ALU = 1;

case (src)

R0: Sel_R0 = 1;

R1: Sel_R1 = 1;

R2: Sel_R2 = 1;

R3: Sel_R3 = 1;

default : err_flag = 1;

endcase

case (dest)

R0: Load_R0 = 1;

R1: Load_R1 = 1;

R2: Load_R2 = 1;

R3: Load_R3 = 1;

default: err_flag = 1;

endcase

end // NOT

RD: begin

next_state = S_rd1;

Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;

end // RD

WR: begin

```

        next_state = S_wr1;
        Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
    end // WR

```

```

BR: begin
    next_state = S_br1;
    Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
end // BR

```

```

BRZ: if (zero == 1)
    begin//Fetching the next instruction without incrementing PC if the condition satis
        next_state = S_br1;
        Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
    end // BRZ
else
    begin //If the condition fails then the code in the next address shouldn't be fetch
        next_state = S_fet1;
        Inc_PC = 1;
    end

```

```

BRO: if (over_flow == 1)
    begin
        next_state = S_br1; //Fetching the next instruction without incrementing PC if
        Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
    // BRZ
    else //If the condition fails then the code in the next address shouldn't be fetched an
        begin
            next_state = S_fet1;
            Inc_PC = 1;
        end

```

```

MULT: begin

```

```

        next_state    = S_ex2 ;
        Sel_Bus_1     = 1      ;
        Load_Reg_Y    = 1      ;
        case (src)
            R0:        Sel_R0 = 1;
            R1:        Sel_R1 = 1;
            R2:        Sel_R2 = 1;
            R3:        Sel_R3 = 1;
            default :   err_flag = 1;

```

```

        endcase
    end // MULT

```

```

    default :
        next_state = S_halt;
    endcase // (opcode)

```

```

S_ex1:      begin

               next_state = S_fet1;
               Load_Reg_Z = 1;
               Load_Reg_ov =      1;      //BRO
               Sel_ALU = 1;
               case (dest)
                   R0: begin Sel_R0 = 1; Load_R0 = 1; end
                   R1: begin Sel_R1 = 1; Load_R1 = 1; end
                   R2: begin Sel_R2 = 1; Load_R2 = 1; end
                   R3: begin Sel_R3 = 1; Load_R3 = 1; end
                   default : err_flag = 1;
               endcase
            end

S_ex2:      begin

               next_state      = mul_done_wait      ;
               //Load_Reg_md      = 1                  ;
               //temp              =~temp;
               case (dest)
                   R0: Sel_R0 = 1;
                   R1: Sel_R1 = 1;
                   R2: Sel_R2 = 1;
                   R3: Sel_R3 = 1;
                   default : err_flag = 1;
               endcase
            end

mul_done_wait:begin

               if(mul_done == 1)
               begin
                   next_state = LD_MUL_MSB          ;
                   Load_Reg_Z   =      1              ;
                   Load_Reg_ov  =      1              ;
                   Sel_mul_LSB = 1                    ;
                   case (src)
                       R0: Load_R0 = 1              ;
                       R1: Load_R1 = 1              ;
                       R2: Load_R2 = 1              ;
                       R3: Load_R3 = 1              ;
                       default : err_flag = 1          ;
                   endcase
               end
               else
               begin
                   next_state      = mul_done_wait      ;
                   Load_Reg_md = 1                  ;
                   temp              =~temp;// for debug

```

```

        case (dest)
            R0: Sel_R0 = 1;
            R1: Sel_R1 = 1;
            R2: Sel_R2 = 1;
            R3: Sel_R3 = 1;
            default : err_flag = 1;
        endcase
    end
end

LD_MUL_MSB: begin
    next_state = S_fet1;
    Load_Reg_Z   = 1;
    Load_Reg_ov  = 1;
    Sel_mul_MSB = 1;
    case (dest)
        R0: Load_R0 = 1;
        R1: Load_R1 = 1;
        R2: Load_R2 = 1;
        R3: Load_R3 = 1;
        default : err_flag = 1;
    endcase
end

S_rd1: begin
    next_state = S_rd2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end

S_wr1: begin
    next_state = S_wr2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end

S_rd2: begin
    next_state = S_fet1;
    Sel_Mem = 1;
    case (dest)
        R0: Load_R0 = 1;
        R1: Load_R1 = 1;
        R2: Load_R2 = 1;
        R3: Load_R3 = 1;
        default : err_flag = 1;
    endcase
end

```

```

                                endcase
                                end

S_wr2:      begin
                                next_state = S_fet1;
                                write = 1;
                                case (src)
                                        R0:      Sel_R0 = 1;
                                        R1:      Sel_R1 = 1;
                                        R2:      Sel_R2 = 1;
                                        R3:      Sel_R3 = 1;
                                        default :   err_flag = 1;
                                endcase
                                end

S_br1:      begin next_state = S_br2; Sel_Mem = 1; Load_Add_R = 1; end
S_br2:      begin next_state = S_fet1; Sel_Mem = 1; Load_PC = 1; end
S_halt:     next_state = S_halt;
default:    next_state = S_idle;

endcase
end

endmodule

```

13) Memory_Unit:

```
module Memory_Unit (data_out, data_in, address, clk, write);
    parameter word_size = 8;
    parameter memory_size = 256;

    output [word_size-1: 0] data_out;
    input [word_size-1: 0] data_in;
    input [word_size-1: 0] address;
    input clk, write;
    reg [word_size-1: 0] memory [memory_size-1: 0];

    assign data_out = memory[address];

    always @ (posedge clk)
        if (write) memory[address] = data_in;

endmodule
```